

Department of Electrical and Computer Engineering

University of Victoria

ELEC 300 - Linear Circuits II

## LABORATORY REPORT

Experiment No.:	4
Title:	Analysis and Applications of Active Networks
Date of experiment:	18 March, 2016
Report submitted on:	25 March, 2016
To:	H. Singh, B07
Names:	M. Drinnan (V00755525) T. Mulligan (V00819591) T. Stephen (V00812021)

# 1 Objective

This experiment will use active, first order circuits to explore s-domain network analysis.

## 2 Introduction

The Laplace transform,  $\mathcal{L}$ , simplifies the analysis of complex networks by replacing network elements with their equivalent impedances. Integro-differential operations in the time-domain become algebraic operations in the Laplace s-domain.

A first order network with an active element can be generalized by the model shown in Fig. 1.

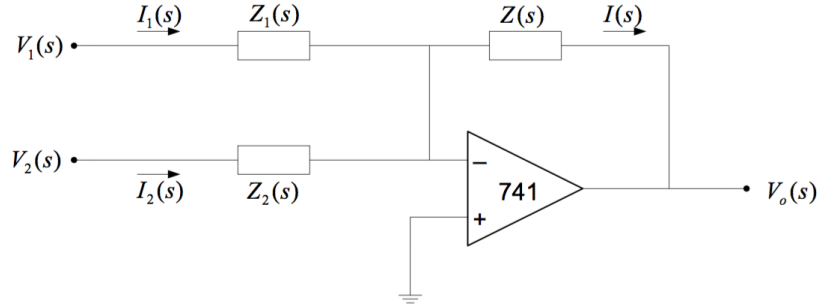


Figure 1: First order network in the s-domain

In the s-domain, the output is

$$V_o = - \left[ \frac{Z}{Z_1} V_1 + \frac{Z}{Z_2} V_2 \right] \quad (1)$$

This general configuration gives rise to many different circuits depending on the values of  $Z$ ,  $Z_1$  and  $Z_2$ .

**Inverting Voltage Amplifier**  $Z = R, Z_1 = R_1, Z_2 = \infty$

$$V_o = - \frac{R}{R_1} V_1 \quad (2)$$

**Inverting Adder**  $Z = R, Z_1 = R_1, Z_2 = R_2$

$$V_o = - \left[ \frac{R}{R_1} V_1 + \frac{R}{R_2} V_2 \right] \quad (3)$$

**Inverting Integrator**  $Z = \frac{1}{sC}$ ,  $Z_1 = R_1$ ,  $Z_2 = \infty$

$$V_o = -\frac{1}{R_1 C} \cdot \frac{1}{s} V_1 = -G_1 \frac{1}{s} V_1 \quad (4)$$

In the time domain this becomes

$$v_o(t) = -G_1 \int_0^t v_1(\tau) d\tau.$$

**Inverting Integrator**  $Z = \frac{1}{sC}$ ,  $Z_1 = R_1$ ,  $Z_2 = R_2$

$$V_o = -\frac{1}{s} \left[ \frac{1}{R_1 C} V_1 + \frac{1}{R_2 C} V_2 \right] \quad (5)$$

### 3 Results

Describe the apparatus and measurement technique(s). Present the data.

### 4 Discussion

Analysis and interpretation of data.

### 5 Conclusion

Justify conclusions and results.