

Department of Electrical and Computer Engineering

University of Victoria

ELEC 300 - Linear Circuits II

## LABORATORY REPORT

Experiment No.:	2
Title:	Frequency response of linear systems
Date of experiment:	19 February, 2016
Report submitted on:	26 February, 2016
To:	TA, B07
Names:	M. Drinnan (V00XXXXXX) T. Mulligan (V00XXXXXX) T. Stephen (V00812021)

## 1 Objective

This experiment will create a type of RC circuit called a *phase lag circuit*. The circuit's transfer function will be used to determine the component values in the circuit for pre-defined frequency responses. The magnitude and phase responses of the circuit will be examined for a range of input frequencies.

## 2 Introduction

$$H(s) = K \frac{s - z}{s - p} \quad (1)$$

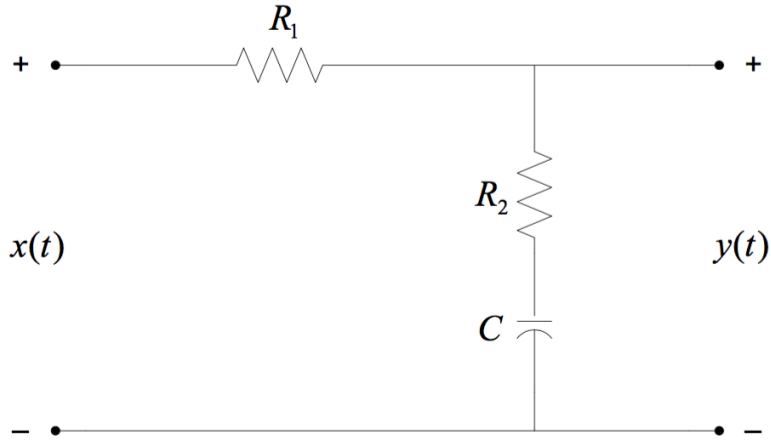


Figure 1: Schematic of a phase lag circuit

For the circuit in Fig. 1, the transfer function is:

$$H(s) = \frac{R_2 + \frac{1}{sC}}{R_1 + R_2 + \frac{1}{sC}} = \frac{R_2}{R_1 + R_2} \frac{s + \frac{1}{CR_2}}{s + \frac{1}{C(R_1 + R_2)}}. \quad (2)$$

Comparing (1) with (2) gives:

$$\begin{aligned} K &= \frac{R_2}{R_1 + R_2} \\ |z| &= \frac{1}{CR_2} \\ |p| &= \frac{1}{C(R_1 + R_2)}. \end{aligned}$$

### 3 Results

$$|H(j\omega)|_{dB} = 20 \times \log \left( \frac{V_y}{V_x} \right) \quad (3)$$

$$\phi_{lag} = \phi_x - \phi_y$$

$f$ (Hz)	$V_y$ (V)	$ H(j\omega) _{dB}$	$\phi_{lag}$ ( $^\circ$ )
----------	-----------	---------------------	---------------------------

Table 1: Response of Fig. 1 to frequency change ( $V_x = 5$  V)

### 4 Discussion

### 5 Conclusion

Justify conclusions and results.